BASIC ELECTRICITY AND ELECTRONICS FOR CONTROL

FUNDAMENTALS AND APPLICATIONS

3rd Edition

by

Lawrence M. Thompson

TABLE OF CONTENTS

PREFACE ..... **XIII**

LIST OF CHAPTER OBJECTIVES ..... **XV**

1 ELECTRICAL BASICS **1**

ENERGY 1
POTENTIAL 1
CHARGE AND CURRENT 3
THE COMPLETE PATH 4
ELECTRICAL UNITS 5
SAFETY 8
VOLTS, AMPS, AND OHMS 9
STEADY VOLTAGE 9
OHM 10
CONCLUSION 16

2 TERMINOLOGY **17**

ACCURACY AND PRECISION 17
LEAST COUNT 19
DIGITAL OR ANALOG 20
REVIEW OF NUMBER SYSTEMS 25
CONCLUSION 33

3 MEASUREMENT ERRORS **35**

ERROR TYPES 35
MORE DEFINITIONS 36
MEAN 37
DEVIATION 38
STANDARD DEVIATION 40
COMPARISON CALIBRATION 41
CALIBRATION CURVES 42
MEASUREMENT UNCERTAINTY 45
MEDIAN AND MEAN 45
UNCERTAINTY 46
CONCLUSION 48

4 BASIC ELECTRICAL MEASUREMENT 51

BASIC SETUP 51
THE RULES 52
OHM'S LAW 55
RESISTORS 59
STANDARD VALUES 64
CONCLUSION 70

5 METER MOVEMENTS 71

METER USE PRECAUTIONS 71
ANALOG METERS 72
METER ACCURACY 74
OHM'S SCALE 75
ANALOG METER CHARACTERISTICS 76
DIGITAL METERS 76
LED DISPLAY 77
LCD DISPLAYS 78
EL DISPLAYS 78
CONCLUSION 79

6 DC VOLTAGE MEASUREMENT 81

THE DC VOLTMETER 81
EXTENDED-RANGE VOLTMETER 83
MULTI-RANGE VOLTMETERS 86
METER SENSITIVITY 93
CALIBRATING VOLTMETERS 95
METER PROTECTION CIRCUITS 96
TRANSIT LOCK 97
ANALOG VERSUS DIGITAL VOLTMETER 98
ACCURACY OF MOVEMENT 98
CONCLUSION 103

7 DC CURRENT MEASUREMENT 105

DC CURRENT METERS 105
MOVING COIL METERS 105
SERIES RESISTORS 107
PARALLEL CURRENT PATHS 107
ASSUMED-VOLTAGE METHOD 109
PROPORTIONAL METHOD 110
RECIPROCAL METHOD 110
COMBINATIONAL CIRCUITS 111
EXTENDED METER RANGES 112

PROPERTIES OF DC CURRENT METERS 114
UNIVERSAL/ARYTRON SHUNT 114
MULTI-RANGE CURRENT METER FACTS 115
AMMETER CALIBRATION 116
COMPARISON CALIBRATION 116
VOLTMETER-PRECISION RESISTOR 117
INDUSTRIAL APPLICATION 117
REVIEW 119
CONCLUSION 123

8 DC BRIDGES 125

WHEATSTONE BRIDGE 125
MULTIPLIER RESISTORS 130
APPLICATION 133
CONCLUSION 136

9 AC FUNDAMENTALS 137

ALTERNATING CURRENT DEFINED 137
ELECTROMAGNETISM 139
FIELD DEFINED 139
SINUSOIDAL WAVE SHAPE 140
ALTERNATING VOLTAGE AND CURRENT 142
VALUES OF ALTERNATING CURRENT 144
RMS ENERGY 145
POWER 146
ELECTROMAGNETIC RADIATIONS 147
CONCLUSION 151

10 AC SOURCE FUNDAMENTALS 153

SIGNAL-FUNCTION GENERATOR 153
CONCLUSION 158

11 THE OSCILLOSCOPE 159

CATHODE RAY TUBE 159
DUAL-TRACE OSCILLOSCOPE 163
OTHER FEATURES 164
OSCILLOSCOPE APPLICATIONS 165
OSCILLOSCOPE CONTROLS 166
DETERMINING FREQUENCY WITH
LISSAJOUS PATTERNS 170
CONCLUSION 175

12 REACTIVE COMPONENTS 177

REACTIVE COMPONENTS 177
CAPACITANCE 177
INDUCTANCE 195
DISCHARGING THE MAGNETIC FIELD 197
INDUCTIVE PHASE RELATIONSHIPS 200
RCL CIRCUITS 202
TRANSFORMERS 204
CONCLUSION 214

13 AC MEASUREMENT 215

RECTIFICATION 215
RECTIFICATION 217
AC METERS 219
HALF-WAVE METERS 223
DIGITAL AC METERS 224
CONSIDERATIONS WHEN USING AC METERS..... 225
CONCLUSION 228

14 SOLID STATE: PRINCIPLES 229

PN JUNCTION 229
LEAD IDENTIFICATION 235
AMPLIFIERS 236
AMPLIFIER TROUBLESHOOTING 239
APPLICATION 240
FIELD-EFFECT TRANSISTORS 241
CONCLUSION 245

15 ZENER DIODES, SCRs, AND TRIACS 247

ZENER DIODES 247
VOLTAGE REGULATION 249
SERIES PASS REGULATOR 249
SILICON-CONTROLLED DEVICES 251
SILICON-CONTROLLED RECTIFIERS 251
DIAC 254
TRIAC 254
SILICON-CONTROLLED SWITCH 257
TROUBLESHOOTING 258
CONCLUSION 260

16 OPERATIONAL AMPLIFIERS 261

BASIC OP-AMP 261
THE DISCRETE OP-AMP CIRCUIT 262
ASSUMPTIONS 264
OPERATION 265
TERMINOLOGY 266
LINEAR OP-AMP CIRCUITS 266
OUTPUT OFFSET VOLTAGES 270
APPLICATION 271
COMPARATORS 271
FUNCTIONAL CIRCUITS 274
CONCLUSION..... 280

17 DIGITAL LOGIC 281

FUNCTIONS 281
STORAGE..... 287
COMPUTATIONAL 289
REPRESENTING BINARY PATTERNS..... 290
APPLICATION 291
CONCLUSION..... 297

18 ANALOG/DIGITAL CONVERSION.....299

THE DECIMAL SYSTEM REVIEW..... 299
THE BINARY SYSTEM 300
THE HEXADECIMAL SYSTEM 301
BINARY CODES 306
ANALOG-TO-DIGITAL CONVERSION 314
SUMMARY 322
CALIBRATION 322
CONCLUSION..... 324

19 INDUSTRIAL APPLICATIONS 325

TWO-WIRE LOOP 325
SOLENOIDS..... 327
UNBALANCED-TO-GROUND CIRCUIT 329
BALANCED-TO-GROUND CIRCUIT..... 330
PROGRAMMABLE LOGIC CONTROLLER (PLC) 331
CONCLUSION..... 332

ANSWERS TO CHAPTER EXERCISES 335

INDEX 373